

Homework 3

Problem 3.1

Solution:

These are the rules I will be using (same as in lecture 3-4 slides) :

- $R1 \rightarrow$ Commutative
- $R2 \rightarrow$ Associative
- $R3 \rightarrow$ Distributive
- $R4 \rightarrow$ Idempotent
- $R5 \rightarrow$ Involution
- $R6 \rightarrow$ Complement
- $R7 \rightarrow$ De Morgan
- $R8 \rightarrow 1 \cdot x = x$ and $0 + x = x$
- $R9 \rightarrow 0w = 0$ and $1 + w = 1$

$$\begin{aligned}
 \text{(a)} \quad x &= (M + N)(\overline{M} + P)(\overline{N} + \overline{P}) \\
 &= ((M + N)\overline{M} + (M + N)P)(\overline{N} + \overline{P}) \quad (R3) \\
 &= (M\overline{M} + N\overline{M} + MP + NP)(\overline{N} + \overline{P}) \quad (R3) \\
 &= (0 + N\overline{M} + MP + NP)(\overline{N} + \overline{P}) \quad (R6) \\
 &= (N\overline{M} + MP + NP)\overline{N} + (N\overline{M} + MP + NP)\overline{P} \quad (R3, R8) \\
 &= N\overline{M}\overline{N} + MP\overline{N} + NP\overline{N} + N\overline{M}\overline{P} + MP\overline{P} + NP\overline{P} \quad (R3, R1) \\
 &= 0\overline{M} + MP\overline{N} + 0 + N\overline{M}\overline{P} + 0 + 0 \quad (R6) \\
 &= MP\overline{N} + N\overline{M}\overline{P} \quad (R8, R9)
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad z &= \overline{A}B\overline{C} + AB\overline{C} + B\overline{C}D = B\overline{C}(\overline{A} + A + D) \quad (R1, R2, R3) \\
 &= B\overline{C}(1 + D) \quad (R6) = B\overline{C} \cdot 1 \quad (R9) = B\overline{C} \quad (R8)
 \end{aligned}$$

$$\text{(c)} \quad x = \overline{(M + N + P)Q} = \overline{(M + N + P)} + \overline{Q} \quad (R7) = \overline{M}\overline{N}\overline{P} + \overline{Q} \quad (R7)$$

$$\begin{aligned}
 \text{(d)} \quad z &= \overline{ABC + DEF} = \overline{ABC} \cdot \overline{DEF} \quad (R7) \\
 &= (\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F}) \quad (R7) \\
 &= \overline{A}(\overline{D} + \overline{E} + \overline{F}) + \overline{B}(\overline{D} + \overline{E} + \overline{F}) + \overline{C}(\overline{D} + \overline{E} + \overline{F}) \quad (R3) \\
 &= \overline{A}\overline{D} + \overline{A}\overline{E} + \overline{A}\overline{F} + \overline{B}\overline{D} + \overline{B}\overline{E} + \overline{B}\overline{F} + \overline{C}\overline{D} + \overline{C}\overline{E} + \overline{C}\overline{F} \quad (R3)
 \end{aligned}$$

$$\begin{aligned}
 \text{(e)} \quad z &= \overline{\overline{A}B + C\overline{D} + EF} = \overline{\overline{A}B} \cdot \overline{C\overline{D}} \cdot \overline{EF} \quad (R7) \\
 &= (\overline{\overline{A}} + \overline{\overline{B}})(\overline{C} + \overline{\overline{D}})(\overline{E} + \overline{F}) \quad (R7) = (\overline{A} + B)(\overline{C} + D)(\overline{E} + \overline{F}) \quad (R5) \\
 &= ((\overline{A} + B)\overline{C} + (\overline{A} + B)D)(\overline{E} + \overline{F}) \quad (R3) \\
 &= (\overline{A} \cdot \overline{C} + B\overline{C} + \overline{A}D + BD)(\overline{E} + \overline{F}) \quad (R3) \\
 &= (\overline{A} \cdot \overline{C} + B\overline{C} + \overline{A}D + BD)\overline{E} + (\overline{A} \cdot \overline{C} + B\overline{C} + \overline{A}D + BD)\overline{F} \quad (R3) \\
 &= \overline{A}\overline{C}\overline{E} + B\overline{C}\overline{E} + \overline{A}D\overline{E} + BD\overline{E} + \overline{A}\overline{C}\overline{F} + B\overline{C}\overline{F} + \overline{A}D\overline{F} + BD\overline{F} \quad (R3)
 \end{aligned}$$

$$\begin{aligned}
 \text{(f)} \quad z &= \overline{\overline{A + B\overline{C}} + D(\overline{E} + \overline{F})} = \overline{\overline{A + B\overline{C}}} \cdot \overline{D(\overline{E} + \overline{F})} \quad (R7) \\
 &= (A + B\overline{C})(\overline{D} + (\overline{E} + \overline{F})) \quad (R5, R7) = (A + B\overline{C})(\overline{D} + \overline{E}F) \quad (R5, R7) \\
 &= (A + B\overline{C})\overline{D} + (A + B\overline{C})\overline{E}F \quad (R3) \\
 &= A\overline{D} + B\overline{C} \cdot \overline{D} + A\overline{E}F + B\overline{C} \cdot \overline{E}F \quad (R3)
 \end{aligned}$$

Problem 3.2

Solution:

We first construct the truth table for the circuit

A	B	C	D	x
0	0	0	0	1
1	0	0	0	1
0	1	0	0	0
0	0	1	0	0
0	0	0	1	1
0	0	1	1	1
0	1	0	1	0
1	0	0	1	1
1	1	0	0	0
0	1	1	0	0
1	0	1	0	0
0	1	1	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

So we get the following K-map (same notation as last time):


	$CD(00)$	$CD(01)$	$CD(11)$	$CD(10)$
$AB(00)$	1	1	1	0
$AB(01)$	0	0	0	0
$AB(11)$	0	0	0	0
$AB(10)$	1	1	0	0

Using K-map to simplify we see there is a quad 1, 2, 13, 14 which results in $\bar{B}\bar{C}$ and a pair 2,3 which results in $\bar{A}\bar{B}D$. Therefore the result is:
 $x = \bar{B}\bar{C} + \bar{A}\bar{B}D$

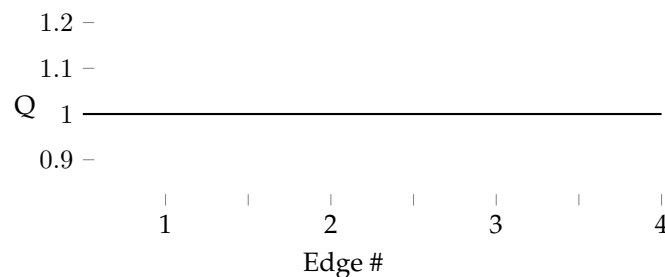Problem 3.3

Solution:

It is given that $Q_0 = 1$. For the given CLK signal, there are 4 positive going edges so we have to check these 4 cases for the value of the output. On the first one, S is 1 and R is 0, which results in a set, so the value of Q stays one. On the second one we have again same values for S and R so Q still stays 1. On the third one the value of S is 0 and the value of R is also 0, which results in the previous state (unchanged) so Q still remains 1. Finally, on the fourth case, S is 1 and R is 0 which results in a set, so Q stays 1. So the waveform for Q will be a straight horizontal line at y=4. So the waveform of Q will be:




So the state table is:

S	R	Output	Edge #	State
1	0	1	1 st ↑	SET
1	0	1	2 nd ↑	SET
0	0	1	3 rd ↑	(no change)
1	0	1	4 th ↑	SET

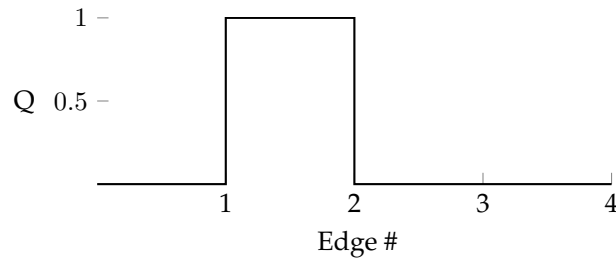Problem 3.4

Solution:

We are given the initial state $Q_0 = 0$. As in the previous case, there are 4 negative going edges so we will see what happens to Q on all 4 of them. On the first one S has a value of 1 and R a value of 0 which as in 3.3 result in a SET so Q becomes 1. On the second one S is 0 and R 1 so we have a RESET therefore Q becomes 0. On the third we see that both S and R are 0 so no change happens and Q still remains 0. Finally on the last one they are again both 0 so the state of Q does not change so it still remains 0. Thus we see a waveform as drawn below:




Now drawing the state table:

S	R	Output	Edge #	State
1	0	1	1 st ↓	SET
0	1	0	2 nd ↓	RESET
0	0	0	3 rd ↓	(no change)
0	0	0	4 th ↓	(no change)

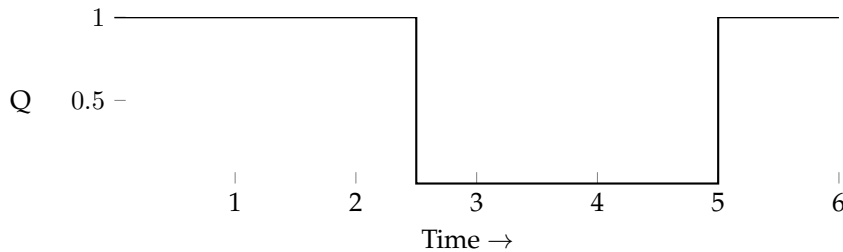Problem 3.5

Solution:

We are given the initial condition of $Q_0 = 1$. We first assume that the hold time is infinitely close to 0. Since for the given CLK waveform there are 6 positive going edges, we need to consider 6 cases. We first notice that for both the first and second case, both J and K are 0, which results in no change, thus Q remains still 1. In the third case, J and K are both 1, which results in a TOGGLE, so Q now becomes 0. In the fourth triggering edge J is 0 and K is 1, which results in a RESET, so Q still remains 0. In the fifth one, J is 1 and K is 0, which results in a SET, so now Q becomes 1. Same case also for the sixth one, J is 1 and K is 0, which results in SET action so Q remains 1.




We calculate the state table as below:

J	K	Output	Edge #	State
0	0	1	1 st ↑	(no change)
0	0	1	2 nd ↑	(no change)
1	1	0	3 rd ↑	TOGGLE
0	1	0	4 th ↑	RESET
1	0	1	5 th ↑	SET
1	0	1	6 th ↑	SET

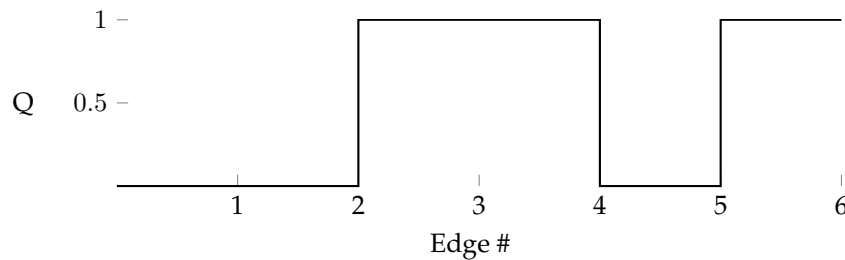Problem 3.6

Solution:

We are given the initial condition of $Q_0 = 0$. As above we first assume that the hold time is infinitely close to 0. Also here we need to consider 6 effective edges in total. For the first one, both J and K are 0 so no change occurs. For both second and third J is 1 and K is 0, which results in SET action, so Q becomes and remains 1. In both fourth and fifth one, both J and K are 1, which results in a TOGGLE action(state), so Q is first toggled to 0 and then again. Finally at the sixth one both J and K are 0, which results in no change at all, so Q still remains 1. So we get the following waveform for Q:



From the reasoning done above the state table is:

J	K	Output	Edge #	State
0	0	0	1 st ↑	(no change)
1	0	1	2 nd ↑	SET
1	0	1	3 rd ↑	SET
1	1	0	4 th ↑	TOOGLE
1	1	1	5 th ↑	TOOGLE
0	0	1	6 th ↑	(no change)

Problem 3.7

Solution:

(a) We want to make $Y = 1$. Since K is connected to the ground it is 0, therefore the only way to achieve what we want is by a SET action, which means we need J to be 1 in the second flip-flop. This means that X has to be 1 and since the first K is also connected to the ground, we want J to also be 1 in the first J-K flip flop so A has to be 1. We also need B and C to be one so that we can see the change, therefore also considering the possible delays of each element, the sequence would be A, B and C.

(b) The initial START pulse is needed to make sure that both X and Y are LOW at the start (It is an asynch. input)

(c) We can use D flip-flops to get a similar circuit (I did my best in the drawing):

